

MAE334 Quiz 8 - November 30th

- 1) What is the zero order uncertainty of a normal analog car speedometer with a $\pm 4\%$ accuracy and 5 MPH gradations at an average speed of 60 MPH?
 - a) ± 2.4 MPH
 - b) ± 2.5 MPH
 - c) ± 4.8 MPH
 - d) ± 5 MPH
 - e) $\pm \sqrt{2.5^2 + 2.4^2}$
- 2) Which of the following are effort variables?
 - a) Temperature
 - b) Velocity
 - c) Pressure
 - d) Heat Flux
 - e) Force
- 3) What is the typical input impedance of a current ADC?
 - a) 10^3 ohms
 - b) 10^4 ohms
 - c) 10^5 ohms
 - d) greater than 10^6 ohms
- 4) A strain gauge should have a very low input impedance?
 - a) True
 - b) False
- 5) An ideal operational amplifier has the following characteristics
 - a) zero input impedance
 - b) infinite input impedance
 - c) infinite gain
 - d) infinite output impedance
 - e) infinite bandwidth
- 6) The gain of standard inverting amplifier pictured here is
 - a) R_1/R_2
 - b) R_2/R_1
 - c) $-R_1/R_2$
 - d) $-R_2/R_1$
 - e) $R_1R_2/(R_1 + R_2)$

